 


ECSE 323 – Digital System Design  
7-Segment LED Decoder  
g39\_7\_segement\_decoder

---

**Description:****Inputs & Outputs:**


code: 4-bit input

mode: 1-bit input

segments\_out : 7-bit output

 **Function:**

A 7-Segment LED Decoder works by taking a 5-bit input (code and mode concatenated) that maps onto an LED segment on the Cyclone II board. The mapping happens according to the diagram below:



For example to generate the shape for the number “0” then we need to light up segments: 0,1,2,3,4 & 5. Since the circuit is an *active low* circuit then that would mean that the input should be “1000000”. This translates to, turn off segment 6, and keep 0 through 5 on. We then proceeded to write the VHDL code for this component using Select “....” When”.....” for all needed inputs.

The circuit operates under 2 modes. Mode 0 is just a normal 4 bit hexadecimal representation, meaning that 0 through 15 would map to 0 through F. Mode 1 is a card face value representation. That means that it maps 0 through 12 to A (Ace) through K (King). Since there are only 13 face values in a deck 13 through 15 maps to “---”.

**Testing:**

Simulation and testing were done on all inputs. Those are 32 valid inputs in total. 16 inputs for mode 0, and 16 inputs for mode 1. Everything was tested and shown to the TA during the demo but below some of those tests are explained:

**Mode 0:**

	Msgs												
st/mode	0												
st/code	1011	0000	0001	0010	0011	0100	0101	0110	0111	1000	1001	1010	1011
st/segments_out	0000011	1000000	1111001	0100100	0110000	0011001	0010010	0000010	1111000	0000000	0010000	0001000	0000011

In this output graph the first line is the mode, as it can be seen by the flat green line, it is at 0 the whole time. The second line is the input code, while the last line is the output of the decoder itself.

As it was explained in the description, input codes map onto certain segments being on/off. The figure above shows inputs 0 to 11. The portion of the VHDL code that controlled this part is the following:

\*Note: the last bit in the input part represents the mode (after concatenation).

```

"1000000" WHEN "00000", -- code = 0, mode = 0
"1111001" WHEN "00010", -- code = 1, mode = 0
"0100100" WHEN "00100", -- code = 2, mode = 0
"0110000" WHEN "00110", -- code = 3, mode = 0
"0011001" WHEN "01000", -- code = 4, mode = 0
"0010010" WHEN "01010", -- code = 5, mode = 0
"0000010" WHEN "01100", -- code = 6, mode = 0
"1111000" WHEN "01110", -- code = 7, mode = 0
"0000000" WHEN "10000", -- code = 8, mode = 0
"0010000" WHEN "10010", -- code = 9, mode = 0
"0001000" WHEN "10100", -- code = 10, mode = 0
"0000011" WHEN "10110", -- code = 11, mode = 0

```

Mode 1:

tst/mode	1												
tst/code	0000	0000	0001	0010	0011	0100	0101	0110	0111	1000	1001	1010	1011
tst/segments_out	0001000	0001000	0100100	0110000	0011001	0010010	0000010	1111000	0000000	0010000	1000000	1100001	0100011

The portion of the VHDL code that controlled this part is the following:

```

"0001000" WHEN "00001", -- code = 0, mode = 1
"0100100" WHEN "00011", -- code = 1, mode = 1
"0110000" WHEN "00101", -- code = 2, mode = 1
"0011001" WHEN "00111", -- code = 3, mode = 1
"0010010" WHEN "01001", -- code = 4, mode = 1
"0000010" WHEN "01011", -- code = 5, mode = 1
"1111000" WHEN "01101", -- code = 6, mode = 1
"0000000" WHEN "01111", -- code = 7, mode = 1
"0010000" WHEN "10001", -- code = 8, mode = 1
"1000000" WHEN "10011", -- code = 9, mode = 1
"1100001" WHEN "10101", -- code = 10, mode = 1
"0100011" WHEN "10111", -- code = 11, mode = 1

```